

FRONTGRADE

APPLICATION NOTE

UT7R995/C

Recommended Bypass Capacitance Values for
the VDD Pins of the UT7R995/C RadClock™

1/1/2007

Version #: 1.0.0

1.0 Overview

The UT7R995 and UT7R995C RadClock are clock buffers with PLL capable of independently driving four banks of outputs to 200 MHz with programmable skews relative to the feedback input. The devices consist of independent power supplies for the core and for each of the four output banks. V_{DD} powers the core, which consists of the PLL, the clock circuitry, and the control logic. There are also independent power supply pins for each output buffer designated as V_{DDQn} ($n:1-4$). The purpose of this application note is to characterize typical current requirements for each power supply and to provide recommended bypass capacitors.

The core and the four output drivers are independent and electrically isolated. Also, the structure of the four output drivers is the same. Therefore, it is sufficient to characterize I_{DD} and one output driver supply I_{DDQn} , where n is either 1, 2, 3 or 4. Channel 3 is selected as the output.

2.0 Lab Setup

In order to characterize the bypass requirements for each V_{DD} pin, it is first necessary to characterize I_{DD} and I_{DDQ3} under controlled conditions. These conditions are captured in Table 1.

Table 1: RadClock Test Configuration

Parameter	Value
Input Frequency	25 MHz
PLL Frequency	50 MHz, 100 MHz, 150 MHz
Load	25pF
Output Drive Level	24mA
VDD	3.3V
V_{DDQ3}	3.3V
Temperature	25oC

The laboratory setup is shown in Figure 1. One side of the 25pF load capacitor is tied to V_{DDQ3} , with the other side soldered to the copper ground plane as shown. To measure I_{DD} or I_{DDQ3} , several capacitors are tied close to the input pins to ensure there is adequate charge needed to supply the ac component of the current. An accoupled current probe is used to monitor the ac component of I_{DD} or I_{DDQ3} .

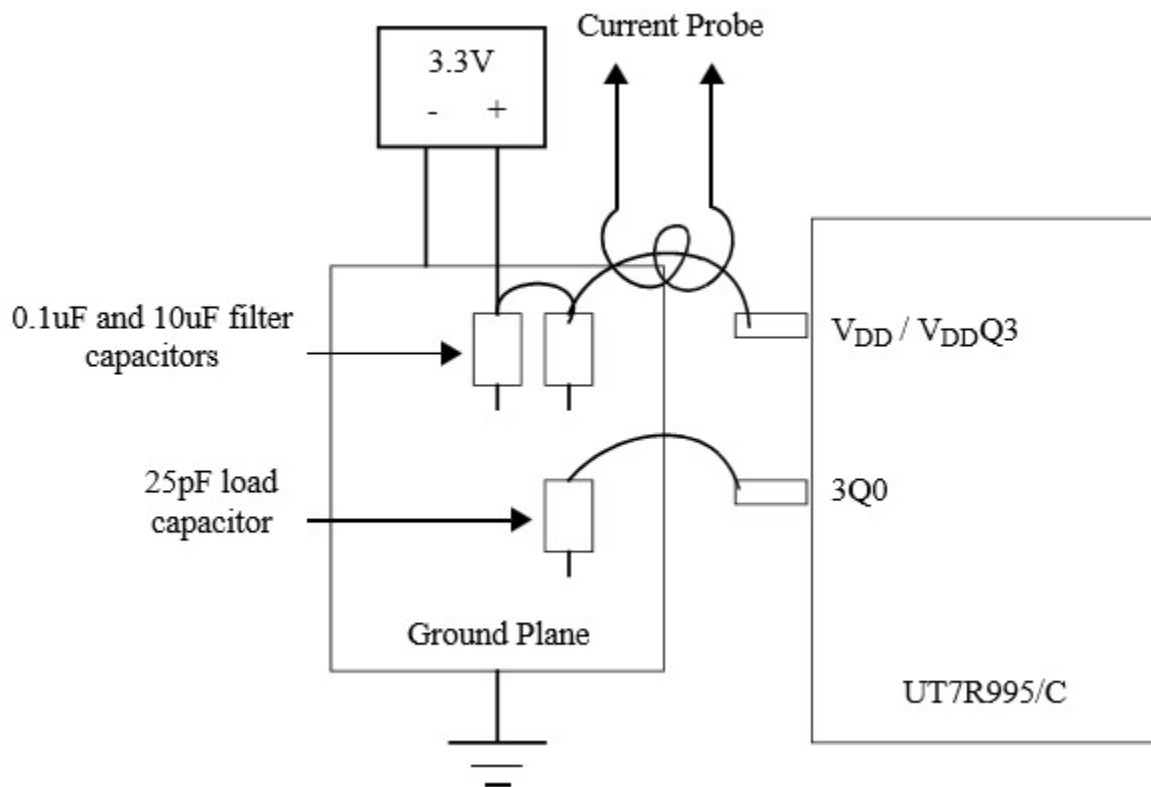


Figure 1. Laboratory Setup for Current Characterization.

In the case where I_{DD} is being measured, V_{DDQ3} is connected normally through the power plane in the PCB. Like- wise, when I_{DDQ3} is being measured, V_{DD} is connected to 3.3V through the PCB. For the I_{DD} measurement, all V_{DD} pins are tied together.

3.0 Lab Results

The input frequency to the UT7R995/C is 25 MHz. The output frequency is set to 50 MHz, 100 MHz, and 150 MHz using the internal PLL divider. Worst-case current for I_{DDQ3} occurs at an output frequency of 50 MHz.

Figure 2 shows the supply current in the top trace where the scale is 5mV/mA. The bottom trace is the output voltage 3Q0, shown for reference. As a first-order approximation, I_{DDQ3} will be modeled as a 100 MHz sine wave. The doubling of frequency in the current waveform relative to the output voltage is due to reflections caused by the capacitive load, as no attempt is made to match the source impedance to the load. The peak-to-peak current is 100mA.

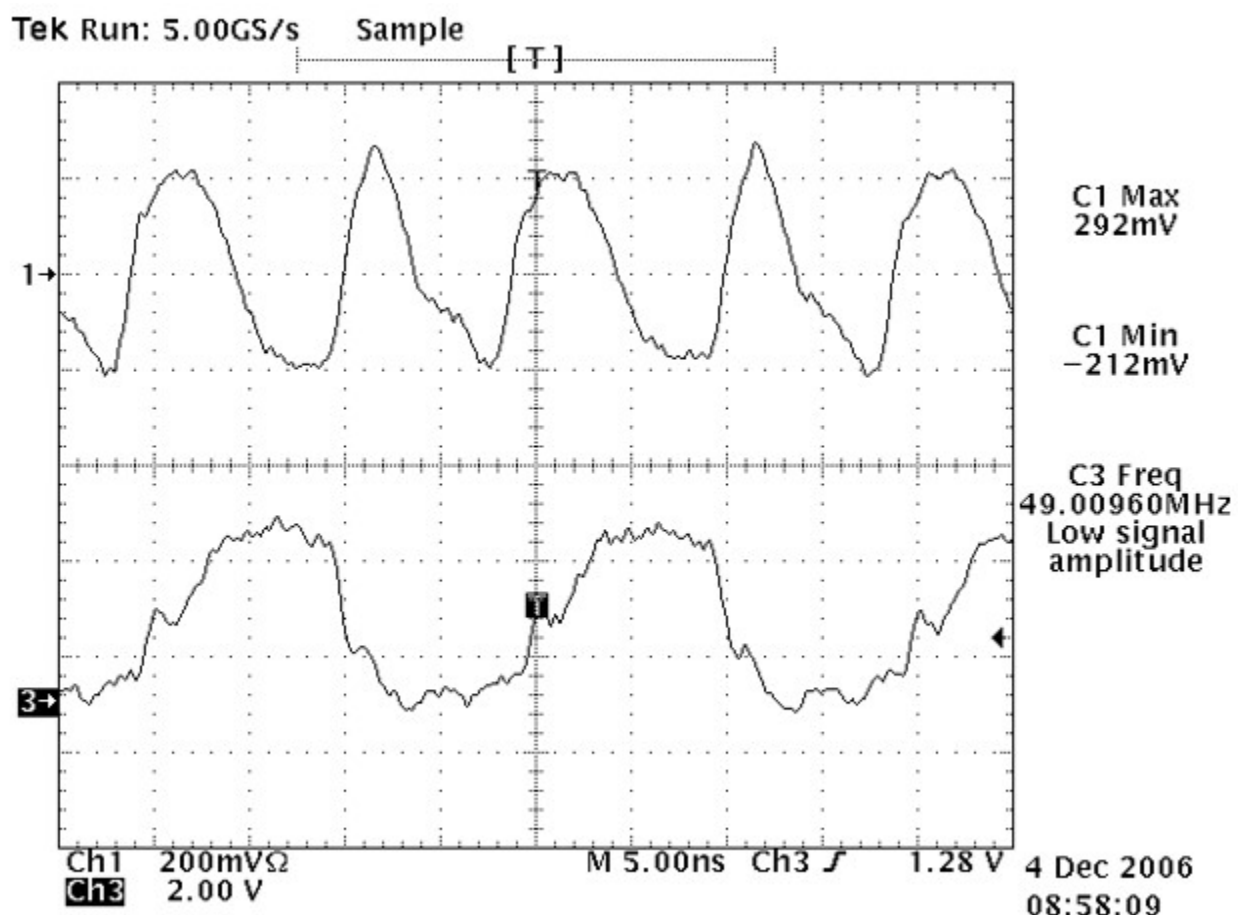


Figure 2. I_{DDQ3} and Output Voltage for Channel 3Q0.

For the core power supply, worst-case I_{DD} occurs at an output frequency of 150 MHz. Figure 3 shows I_{DD} in the top trace where the scale factor is 1mV/mA. The bottom trace is the output voltage 3Q0, shown for reference. The peak-to-peak current is 53mA and is approximated as a sine wave at 150 MHz.

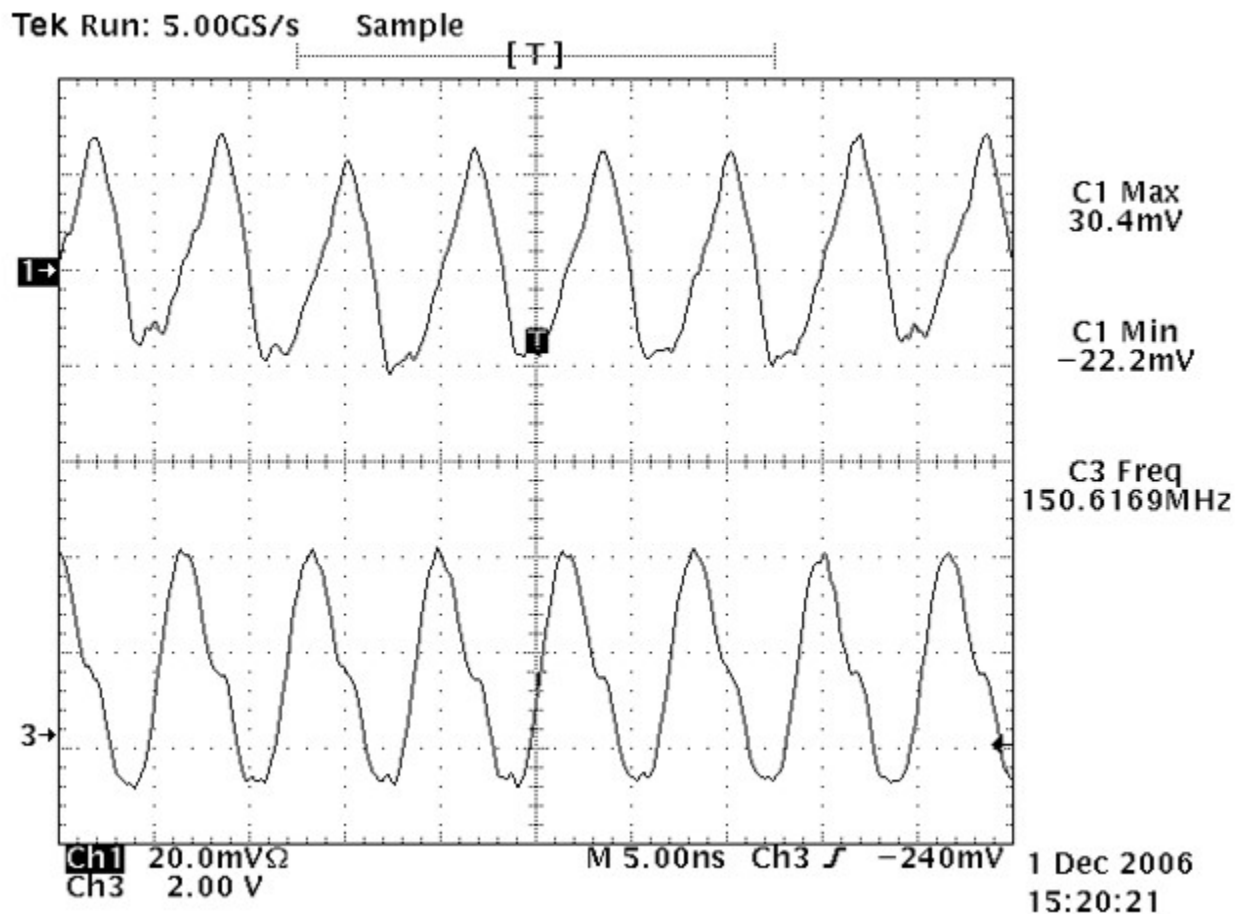


Figure 3. I_{DD} and Output Voltage for Channel 3Q0.

4.0 Simulation Results

The voltage seen at the supply pin is derived by simulating a circuit using the models for the current waveforms shown in Section 3.0. The voltage source is an ideal 3.3V dc source separated from the UT7R995/C power pins by 15cm traces represented by a 150nH inductor and 25m Ω resistor on both sides of the power supply. This represents a worst-case scenario where there is no ground plane and where the voltage regulator is located some distance from the UT7R995/C. A capacitor is placed directly on the power pin whose ESR is determined by assuming a 2.5% dissipation factor, typical for ceramic multi-layer chip capacitors. The circuit is simulated and the ripple voltage on the power pin is determined. Tables 2 and 3 show the ripple voltage with several different capacitor values.

Table 2: Peak-to-Peak Ripple Voltage for VDDQ3

Capacitance	ESR	Ripple Voltage (Vp-p)
0.001uF	40m Ω	140mV
0.01uF	4m Ω	10mV
0.1uF	0.4m Ω	1.6mV

Table 3: Peak-to-Peak Ripple Voltage for VDD

Capacitance	ESR	Ripple Voltage (Vp-p)
0.001uF	26m Ω	55mV
0.01uF	2.6m Ω	5.5mV
0.1uF	0.26m Ω	0.6mV

5.0 Conclusion

In order to minimize ripple voltage, a 0.1uF capacitor should be placed on each V_{DD} and V_{DDQn} input, as close to the pin as possible. V_{DD} pins that are close together may share a bypass capacitor, but V_{DD} should be isolated from the V_{DDQn} inputs. Use of the recommended bypass capacitors will reduce only the ripple voltage due to the ac component of the supply current. The designer should use additional filtering as required to reduce the coupling of transients within the system or due to neighboring components.

Revision History

Date	Revision #	Author	Change Description	Page #

Frontgrade Technologies Proprietary Information Frontgrade Technologies (Frontgrade or Company) reserves the right to make changes to any products and services described herein at any time without notice. Consult a Frontgrade sales representative to verify that the information contained herein is current before using the product described herein. Frontgrade does not assume any responsibility or liability arising out of the application or use of any product or service described herein, except as expressly agreed to in writing by the Company; nor does the purchase, lease, or use of a product or service convey a license to any patents, rights, copyrights, trademark rights, or any other intellectual property rights of the Company or any third party.